

Hardwareentwicklung

HWE

Heinzle Moritz — 07 October 2026

Contents

1 Diferentiator	2
-----------------------	---

1 Diferentiator

07.10.2026

$$f = 1\text{kHz}$$

$$U_S = 2\text{V}$$

$$T = \frac{1}{f} = 1\text{ms}$$

$$\frac{dv_{e(t)}}{dt} = \frac{2}{0.5E - 3} = 4000 \frac{\text{V}}{\text{s}}$$